


Karnatak Science college ,Dharwad
Dept of Physics/Electronics
B.Sc V Semester(NEP)
Electronics Paper I,
Electronics communication II,
Lab Manual
Course Code :035ELE012

Experiment: BENDING LOSSES IN OPTICAL FIBER

AIM: To study the optical losses in fiber by bending the fiber .

APPARATUS: OPTICAL FIBER KIT, Different size bends ,DMM.

DIAGRAM:

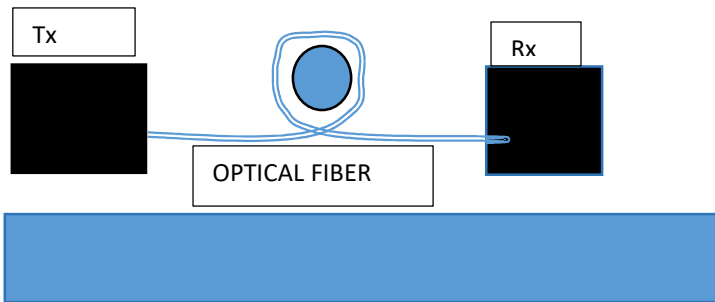

TABULAR COLUMN:

SL NO	BEND SIZE in cm	OUTPUT VOLTAGE in volt

RESULT:

Experiment : Numerical Aperture of Given OFC

Aim: Study the numerical aperture of given optical fiber(OFC).

Apparatus: OFC, Light source(LED or LASER), Scale.


Formula:

$$\text{Numerical Aperture(NA)} = \frac{R}{\sqrt{R^2 + L^2}}$$

Where R=Radius of the circle fully focused in cm.

L= Distance between moving scale and OFC on fixed plate in cm.

Diagram:

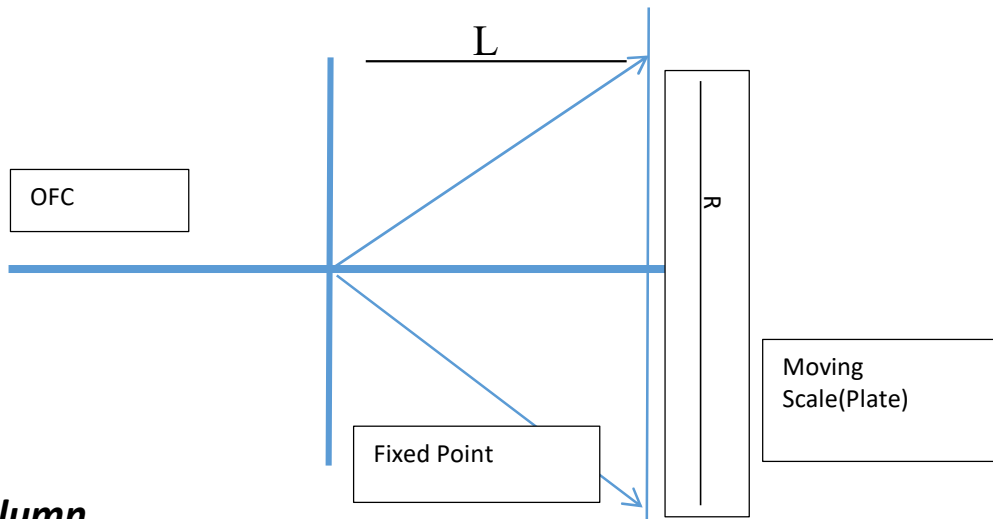

Tabular column

SL NO	Diameter of circle fully covered" D" (cm)	R=D/2 In cm	Distance between OFC and plate L(cm)	NA = $\frac{R}{\sqrt{R^2 + L^2}}$	Mean NA	$\sin^{-1} (NA)$

Result:

Experiment :Frequency response of OFC

Aim:To study the Relationship between the input signal and output (Received)signal i,e Frequency response of optical fiber link.

Apparatus:CRO, Optical fiber kit,Chords,Power supply.


Formula:

$$\text{Gain} = V_{\text{out}} / V_{\text{in}}$$

Where V_{out} =Output voltage

V_{in} = Input voltage

Nature of graph:

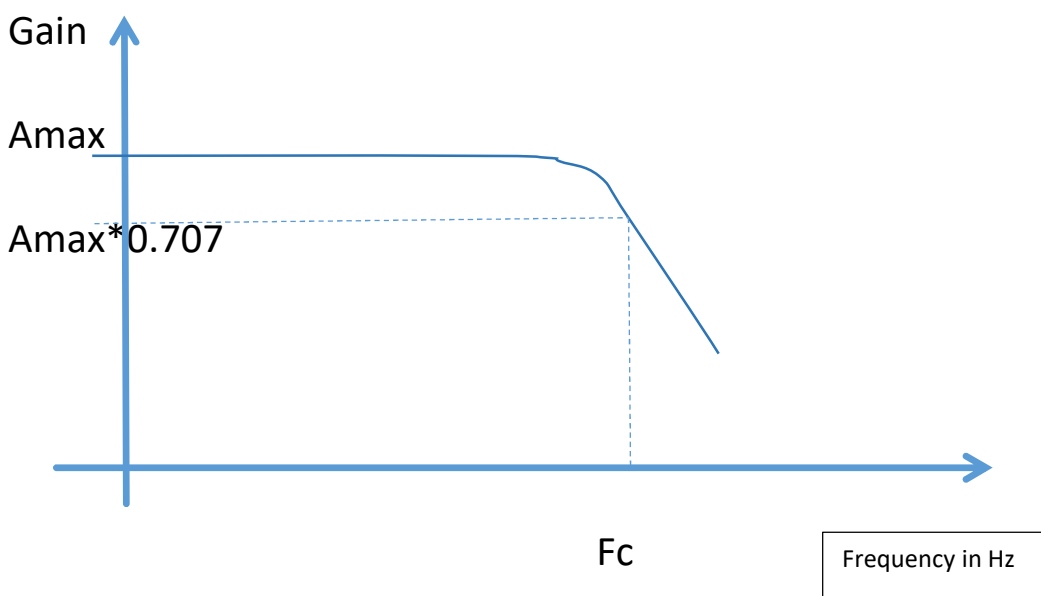

Observations:

Frequency f in Hz	Input Voltage(Vin) in Volt	OutputVoltage(Vout) in Volt	Gain=Vout/Vin

Result:

Experiment :CLASS C TUNED AMPLIFIER


AIM:To design and test a class c tuned amplifier to work at the given frequency and to determine its cut-off frequency.

APPARATUS: Power Supply,Function Generator,AC milli-voltmeter or CRO,Transistor,Resistors, Capacitors, Connecting wires.


FORMULA: Cut-off Frequency

$$f_c = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

NATURE OF GRAPH:

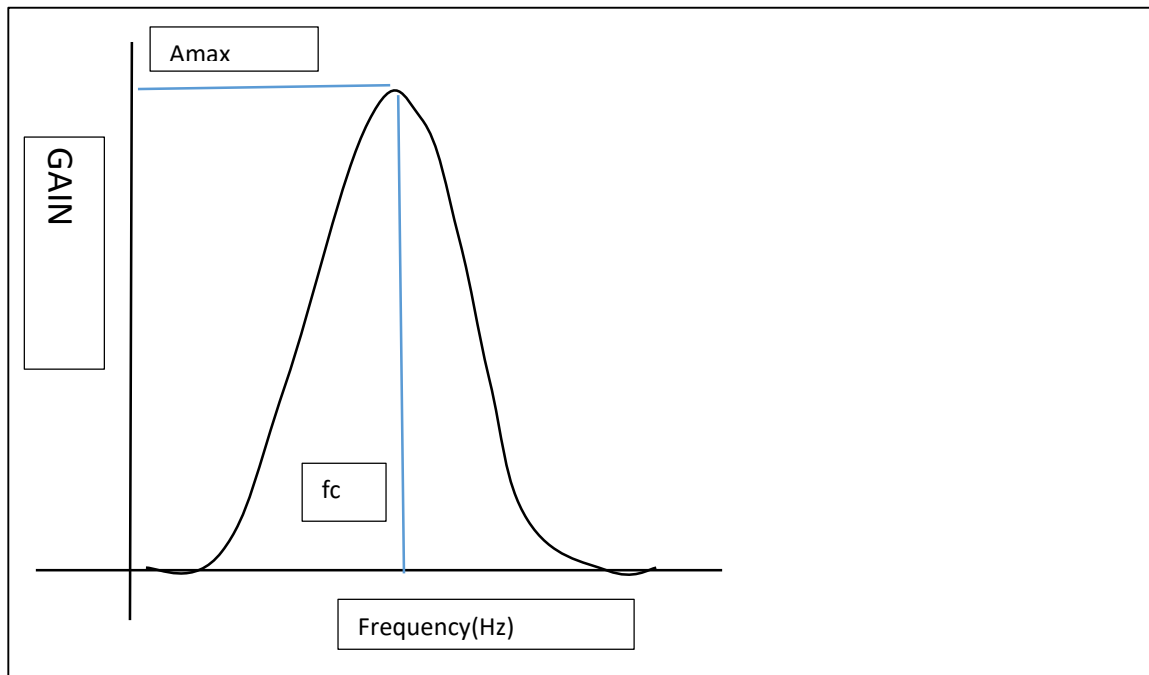

CIRCUIT DIAGRAM:

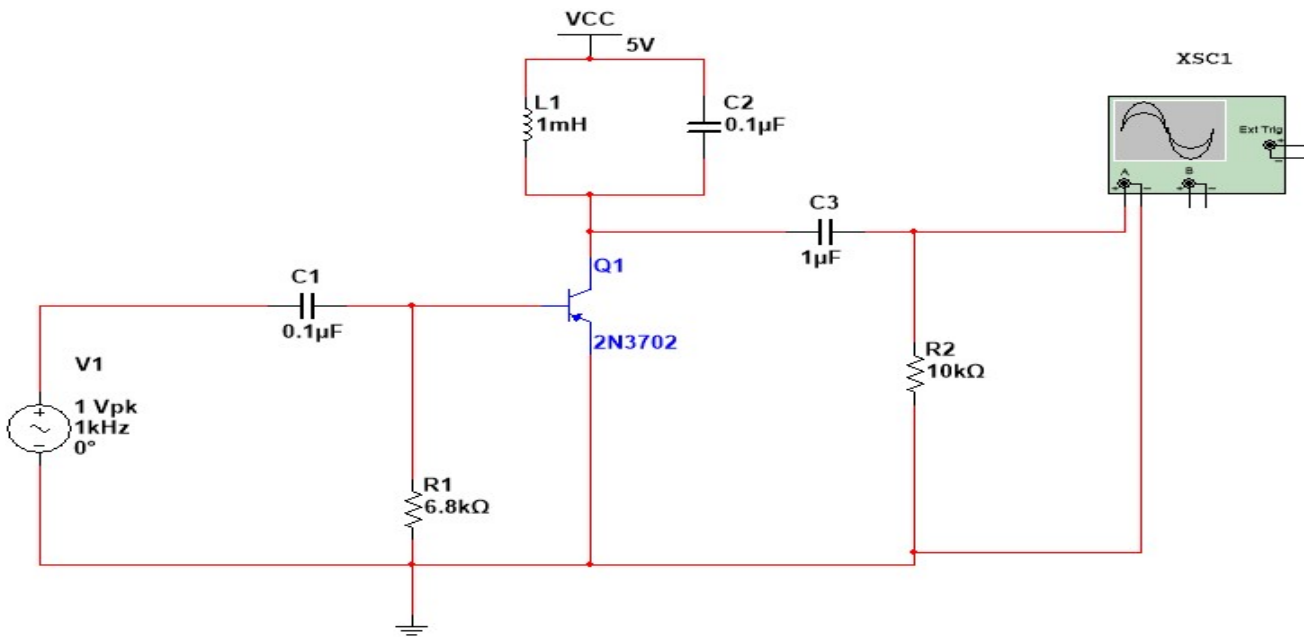

TABULAR COLUMN

L=.....H C=.....F fc=.....Hz

Frequency in Hz	Input voltage (Vin) V	Output voltage (Vout) V	Gain=Vout/Vin

RESULT:

Experiment :Active Low Pass Filter

Aim:To design active low pass filter and to obtain the frequency of the active low pass filter.

Apparatus: Capacitors,Resisters,OP-AMP(IC-741), Dual Power supply, AC millivoltmeter,Signal Generator.

Formula:

- For First Order Low pass filter

$$f_c = \frac{1}{2\pi RC} \text{ Hz}$$

- For Second Order Low pass filter

$$f_c = \frac{1}{2\pi\sqrt{R_1R_2C_1C_2}} \text{ Hz}$$


If $R_1=R_2=R$, $C_1=C_2=C$

Then $f_c = \frac{1}{2\pi RC} \text{ Hz}$


- Gain $A_v = 1 + \frac{R_f}{R_1}$

Circuit Diagram


First order Low pass filter

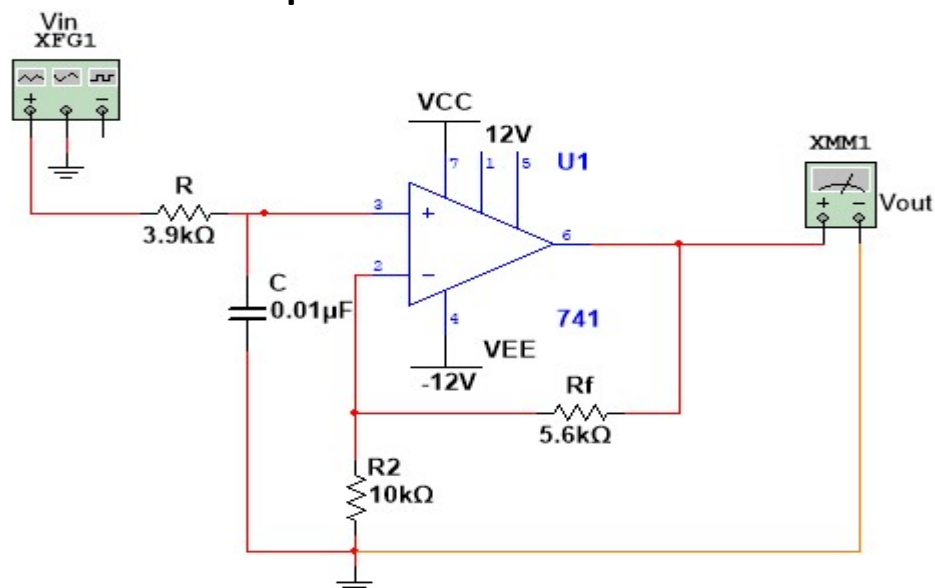

Second order Low pass filter

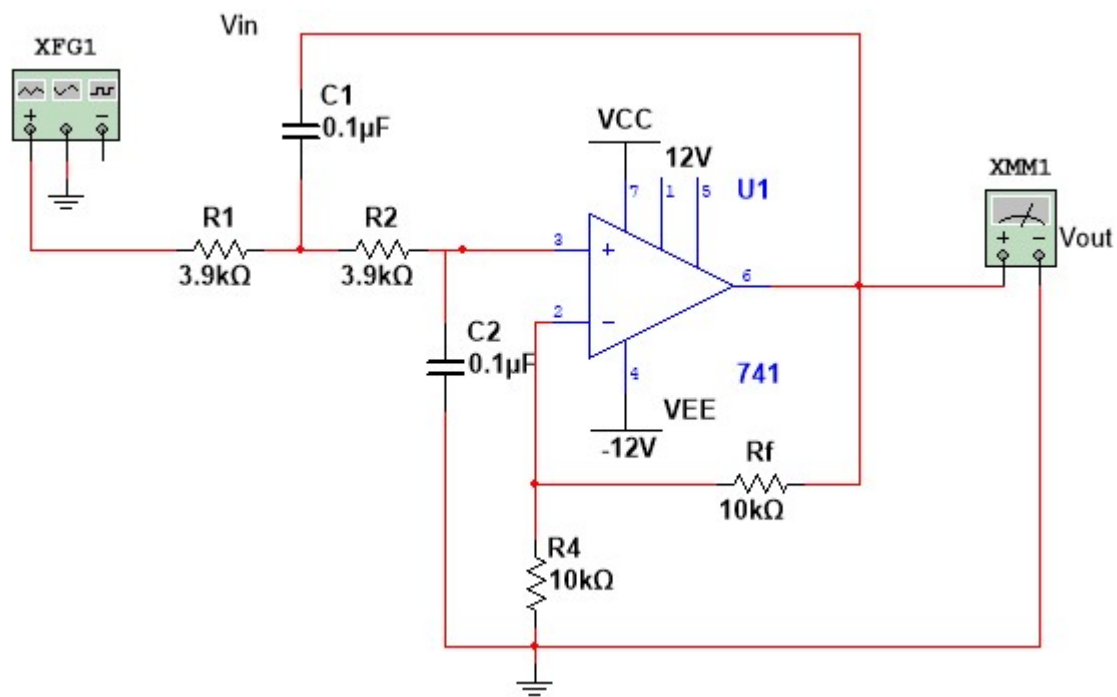

Nature of Graph

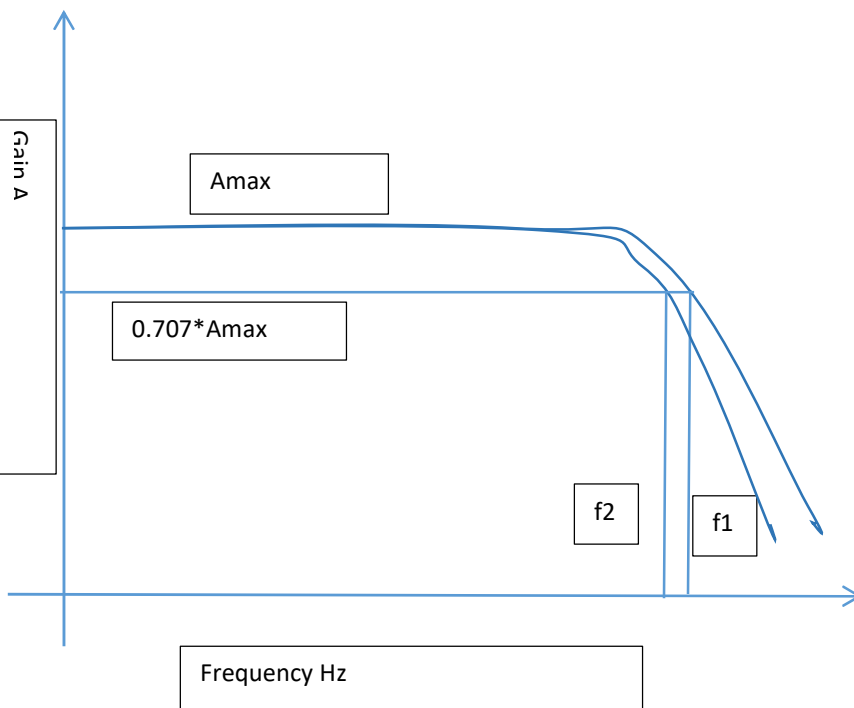

f 1=High frequency

F 2=Low frequency

Tabular column

Input voltage, V_{in} = V

Input Frequency = Hz

First order Low pass filter

Frequency in Hz	Output voltage $V_{out}(V)$	Gain(A)= V_{out}/V_{in}

Second order Low pass filter

Frequency in Hz	Output voltage $V_{out}(V)$	Gain(A)= V_{out}/V_{in}

Result:

Experiment :Frequency Multiplier

Aim:To design and setup a Frequency multiplier circuit using OP-AMP to multiply an input frequency by a factor N(i.e N=2).


Apparatus: Capacitors,Resisters,OP-AMP(IC-741), Dual Power supply, CRO,Signal Generator.

Formula:

Output Frequency=2*input frequency

$F_{out}=2 \cdot F_{in}$ Hz

Circuit Diagram

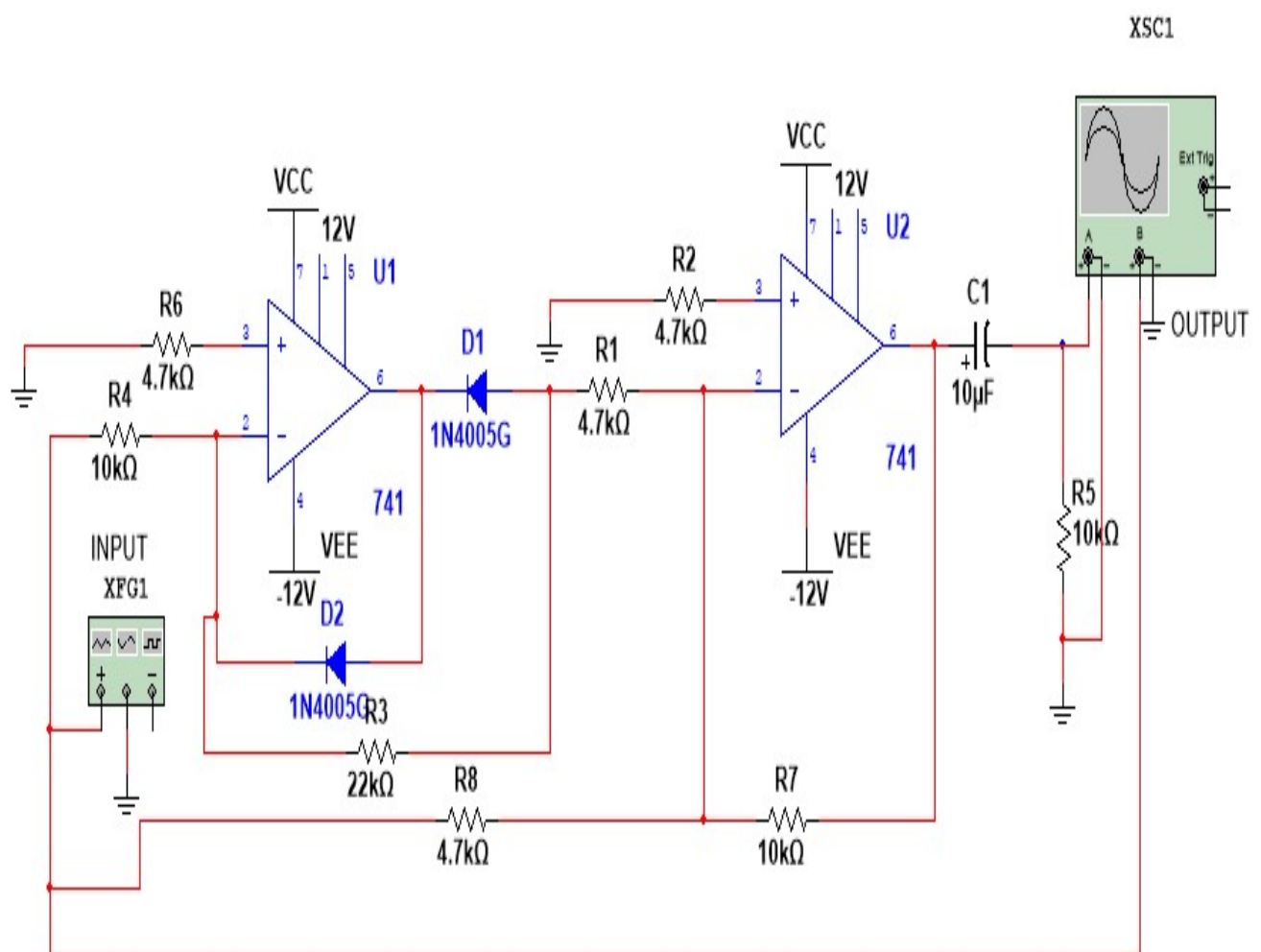

Tabular column

Input Frequency		Output Frequency $F_{out}=2 \cdot F_{in}$ Hz			
SL NO	F_{in} in Hz	No of div(a)	Time/div (b) sec	Time $T=a \cdot b$ sec	$F_{out}=1/T$ Hz

Result:

Experiment :Study of Notch filter

Aim:To design and setup a Notch filter and Study the Frequency of the Notch filter.

Apparatus: Capacitors,Resisters,OP-AMP(IC-741), Dual Power supply, AC millivoltmeter,Signal Generator.

Formula:

- Notch Frequency

$$f_N = \frac{1}{2\pi RC} \text{ Hz}$$


- Gain $A_v = \frac{V_{out}}{V_{in}}$

- Bandwidth= $BW=f_L-f_H$ Hz

f_L =Lower cut off frequency


f_H =Higher cut off frequency

Circuit Diagram

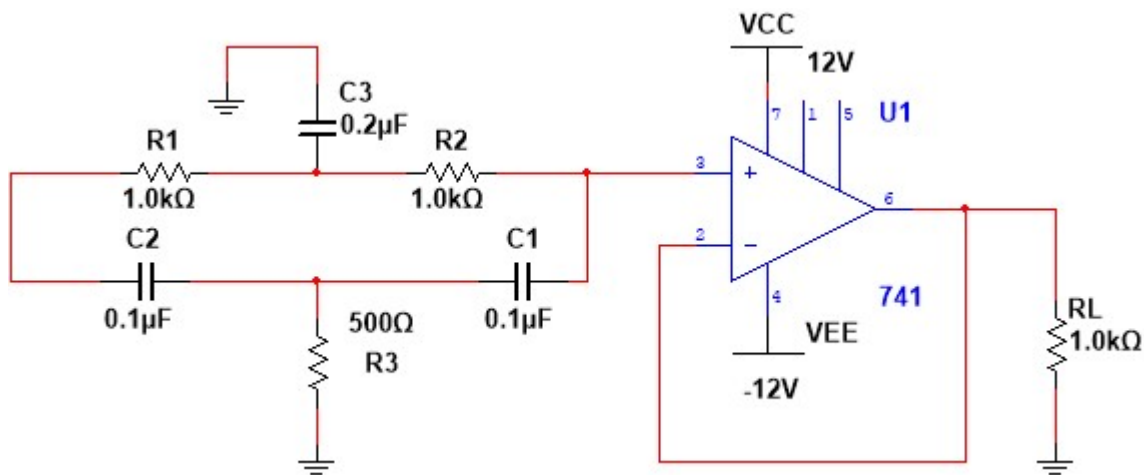

$R1=R2=1K\Omega$. $R3=500\Omega$ $C1=C2=0.1\mu F$ $C3=0.2\mu F$

Nature of Graph

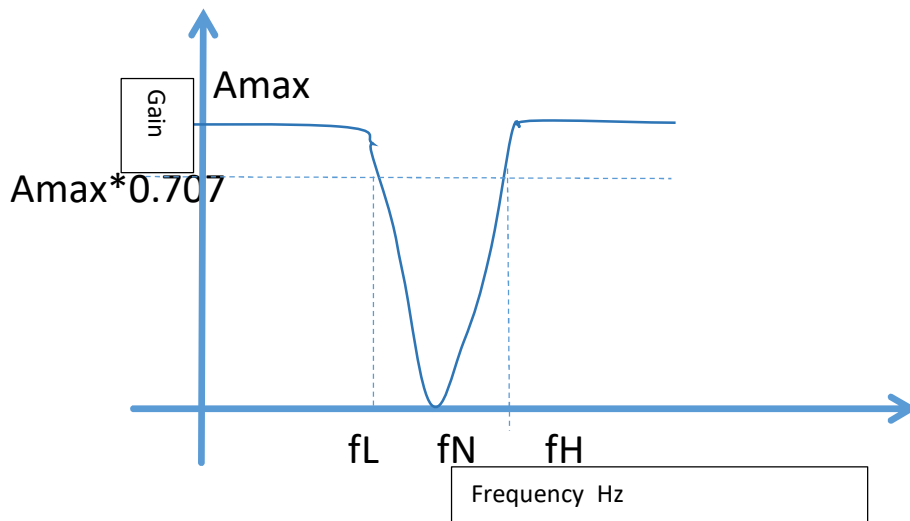

Tabular column

Input Frequency = Hz

Frequency in Hz	Input voltage $V_{in}(V)$	Output voltage $V_{out}(V)$	Gain(A)= V_{out}/V_{in}

Result:


Experiment :Diode Clamping

Aim:Set up semiconductor diode as clamping circuits. Study biased and unbiased circuits. Draw the input and output waveforms for these circuits.

Apparatus: Capacitors, Diodes, Power supply, CRO,Signal Generator.


Circuit Diagram and Tabular column

1) Positive Clamping without bias.

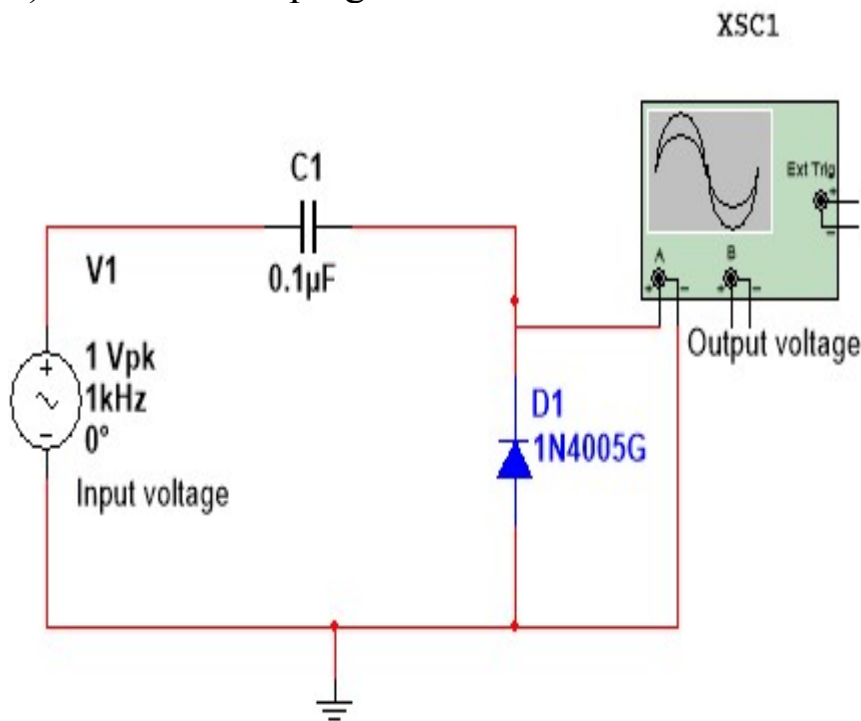


Peak voltage of I/P in Vp(v)	Shift in waveform div(A)	O/P in	Volts/div (B)	Clamped voltage $V=A*B$ in v	Voltage Across Capacitor $V_c=V_p-V_b$ in v

2) Positive Clamping with bias voltage.

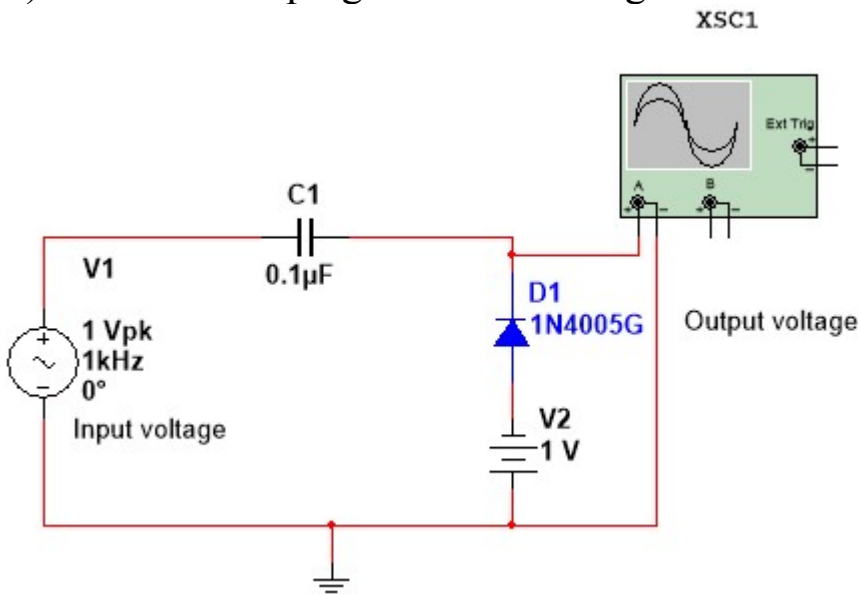


Peak voltage of I/P in Vp(v)	External bias voltage Ve in v	Shift in O/P waveform in div(A)	Volts/div (B)	Clamped voltage V=A*B in v	Voltage Across Capacitor Vc=Vp-Ve-Vb in v

3) Negative Clamping without bias.

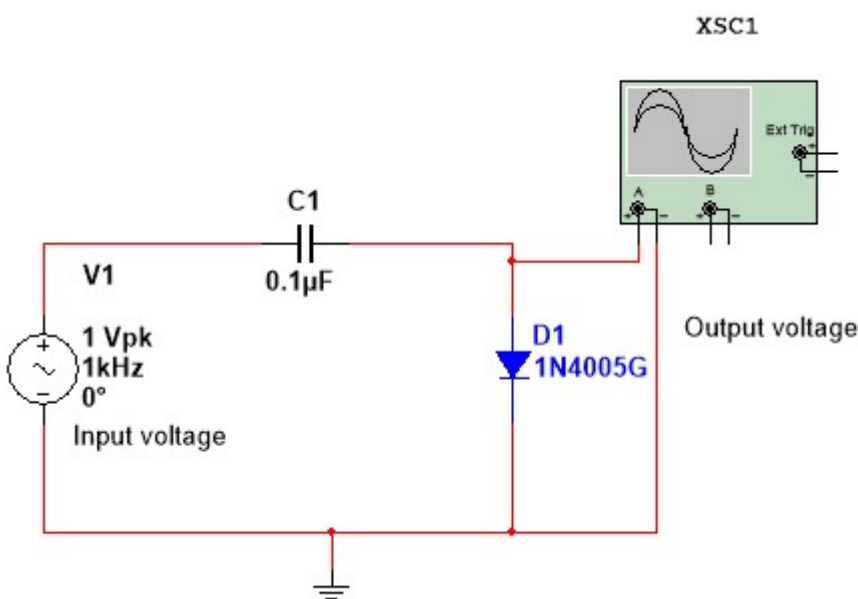

Peak voltage of I/P in $V_p(v)$	Shift in waveform div(A)	O/P in	Volts/div (B)	Clamped voltage $V=A*B$ in v	Voltage Across Capacitor $V_c=V_p-V_b$ in v

4) Negative Clamping with bias voltage.

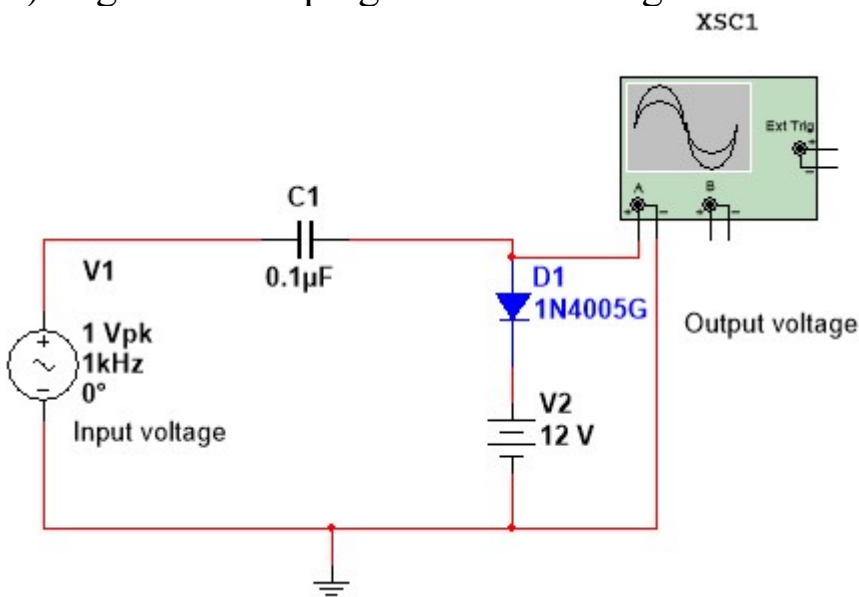

Peak voltage of I/P in $V_p(v)$	External bias voltage V_e in v	Shift in O/P waveform in div(A)	Volts/div (B)	Clamped voltage $V=A*B$ in v	Voltage Across Capacitor $V_c=V_p-V_e-V_b$ in v

Result: